

# KEY

**ECE 210 Final Exam**

**Fall 2000**

Name:


Honor Code:

Instructions:

- ◆ Complete the 4 problems in the allotted time.
- ◆ Use the space on the accompanying pages to work the problems. Do not use a bluebook. Attach additional worksheets if necessary.
- ◆ If you wish to have partial credit awarded for any of your incorrect answers **you must write clearly and legibly**. Explain your work in words, if necessary.
- ◆ Don't Panic.

Good Luck.

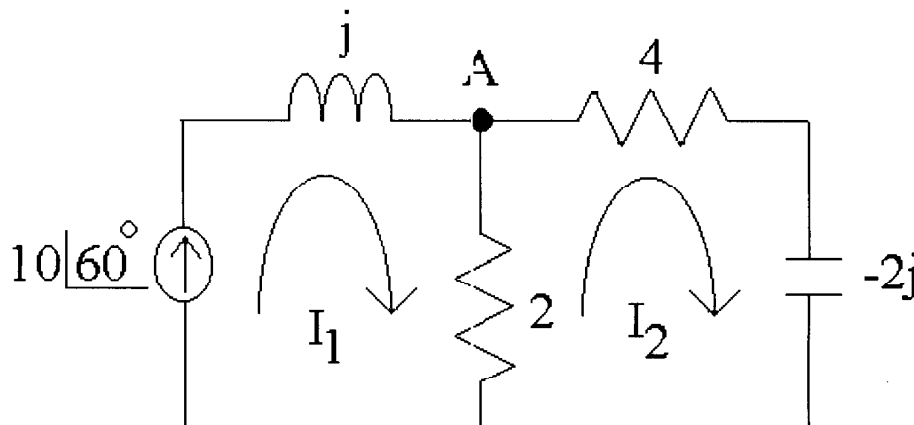1. [21 points] For the circuit below,
  - a. [4+4 points] Solve for A using nodal equation(s).
  - b. [4+4 points] Solve for A using loop equation(s).
  - c. [5] Find the Power Absorbed/Delivered to each of the elements.



$$a. \quad -10 \angle 60^\circ + \frac{A}{2} + \frac{A}{4-2j} = 0$$

$$\Rightarrow \underline{A} = \underline{14.1421 \angle 51.87^\circ} \text{ V}$$

$$b. \quad \underline{I_1} = 10 \angle 60^\circ$$

$$-2(\underline{I_1} - \underline{I_2}) + 4\underline{I_2} - 2j\underline{I_2} = 0$$

$$\underline{I_2} = 3.1623 \angle 78.4^\circ \text{ A}$$

$$\underline{A} = (4-2j)\underline{I_2} = \underline{14.142 \angle 51.87^\circ} \text{ V}$$


$$c. \quad \left. \begin{array}{l} \overline{P_j} = 0 \text{ W} \\ \overline{P_{-2j}} = 0 \text{ W} \end{array} \right\} \text{ Always!}$$

$$P_{2\Omega} = \frac{1}{2} V_m^2 / R = \left(\frac{1}{2}\right) (14.142^2) / 2 = \underline{50 \text{ W}}$$

$$P_{4\Omega} = \frac{1}{2} I_m^2 R = \left(\frac{1}{2}\right) (3.1623)^2 4 = \underline{20 \text{ W}}$$

$$P_{10\angle 60^\circ} = \underline{-70 \text{ W}} \quad \text{since} \quad \underline{\sum_i P = 0}$$

2. [12+8] Find the Voltage  $V_{out}$ .

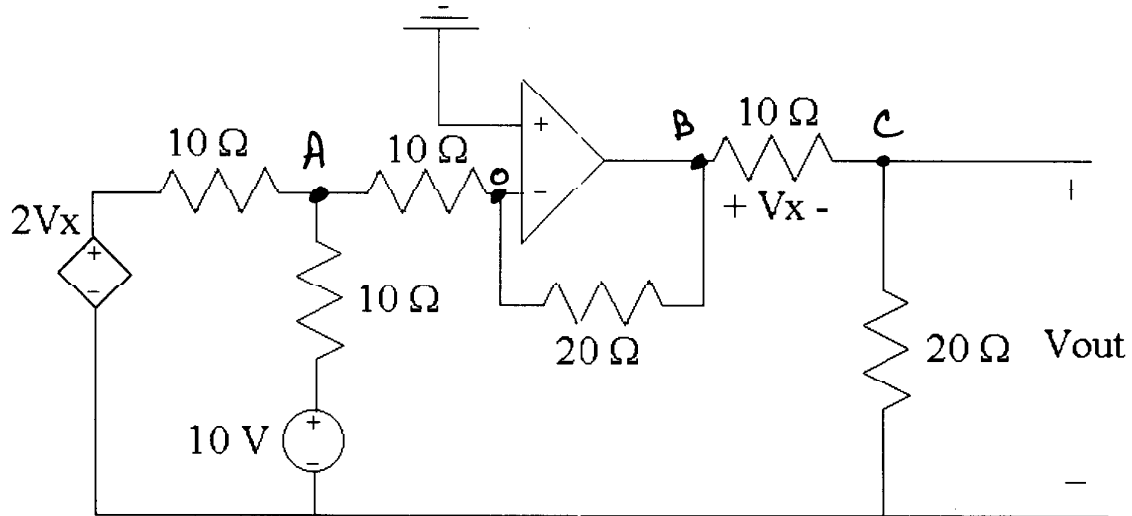

$$\frac{A - 2V_x}{10} + \frac{A - 10}{10} + \frac{A - 0}{10} = 0 \Rightarrow 3A - 2V_x = 10$$

$$\frac{0 - A}{10} + \frac{0 - B}{20} = 0 \Rightarrow 2A + B = 0$$

$$\frac{C - B}{10} + \frac{C}{20} = 0 \Rightarrow 3C - 2B = 0$$

$$V_x = B - C \Rightarrow B - C - V_x = 0$$

4 eqns. 4 unknowns


$$\underline{C = -\frac{40}{13} \text{ V}}$$

3. [25] Choose the best answer.


i. [2] A circuit with sinusoidal input always produces a sinusoidal output.

- a. True  
 b. False

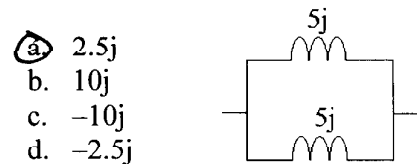
ii. [2] The equivalent single impedance of the following elements is



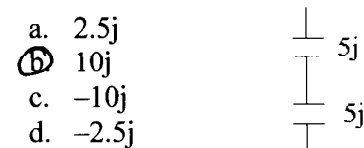iii. [2] The equivalent single impedance of the following elements is



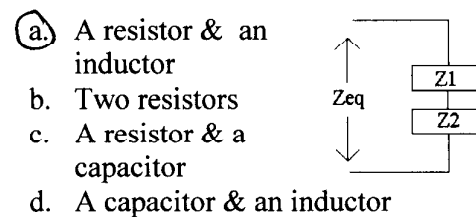iv. [2] The equivalent impedance ( $Z_{eq}$ ) of the two elements  $Z_1$  and  $Z_2$  is  $(20+j10)$  Ohms. They must be:



v. [2] 'Transient response' is


a. The response of a circuit after a 'long' time (as  $t \rightarrow \infty$ )

b. The short-lasting response of a circuit immediately after the power is connected

c. Is only meaningful with DC inputs


d. Both b & c

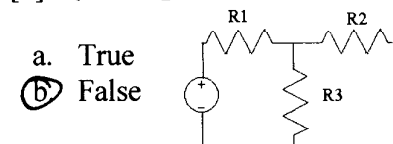vi. [2]  $R_1$  and  $R_2$  are in series.



vii. [2] The steady-state current  $I_o$  is

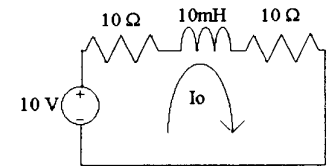- a. 1 A  
b.  $5j$  A  
c.  $10\angle 0^\circ$  A  
 d. 5 A




viii. [2] A circuit with DC input produces an output of the form  $V_{out} = (K_1 - K_2e^{-t/\tau})$

- a. True  
 b. False

ix. [2] The steady-state voltage  $V_o$  is

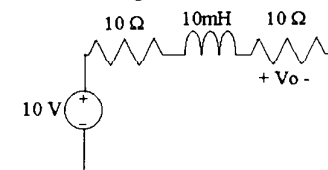
- a.  $e^{-5t}$  V  
b.  $10\angle 0^\circ$  V  
 c. 5 V  
d. 5j V



x. [2] An AC circuit excited by a source with  $\omega=100$  Hz may produce an output with  $\omega=200$  Hz

- a. True  
 b. False

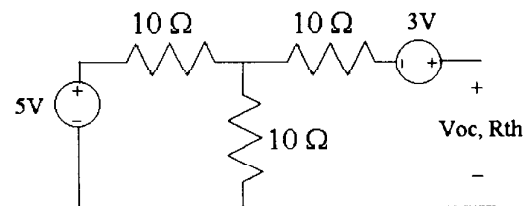xi. [2] The Thevenin equivalent impedance in the following circuit is



- a.  $10 \Omega$   
b.  $5 \Omega$   
 c.  $15 \Omega$   
d.  $50/5 \Omega$

xii. [3] The Thevenin equivalent voltage in the preceding circuit is

- a. 2.5 Volts  
 b. 5.5 Volts  
c. 5 Volts  
d. -0.5 Volts

4. [20 points]
- [8 points] Find  $V_o$  in Fig 4-a.
  - [8 points] Find  $I_o$  in Fig 4-b.
  - [4 points] Find  $R_{th}$  in Fig 4-c.

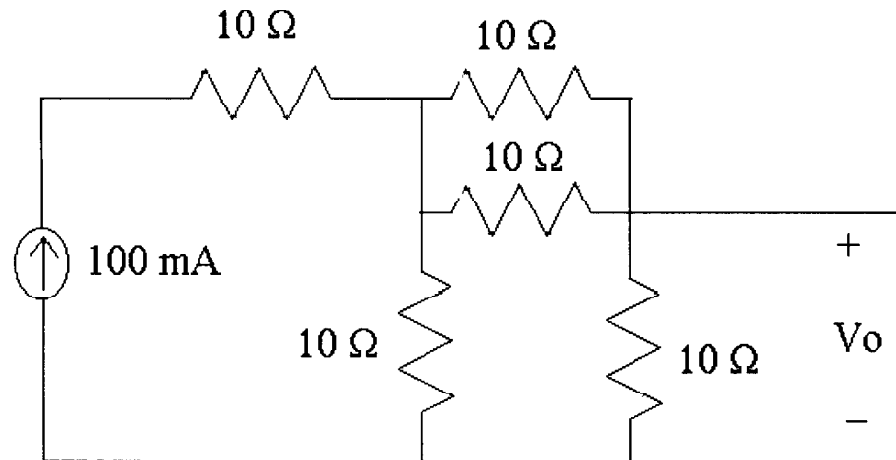


Figure 4-a.

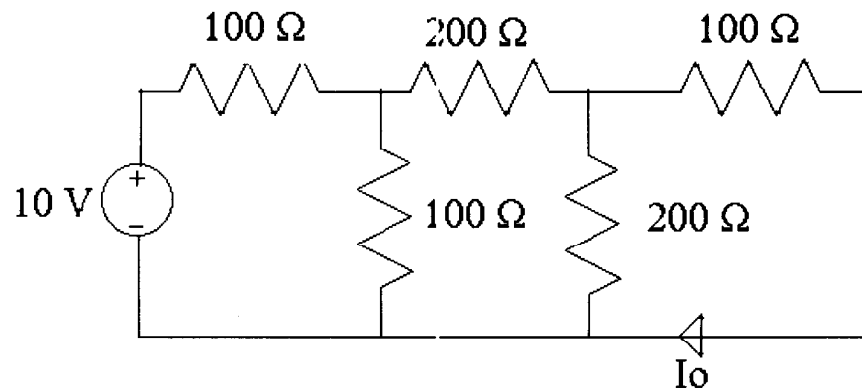


Figure 4-b.


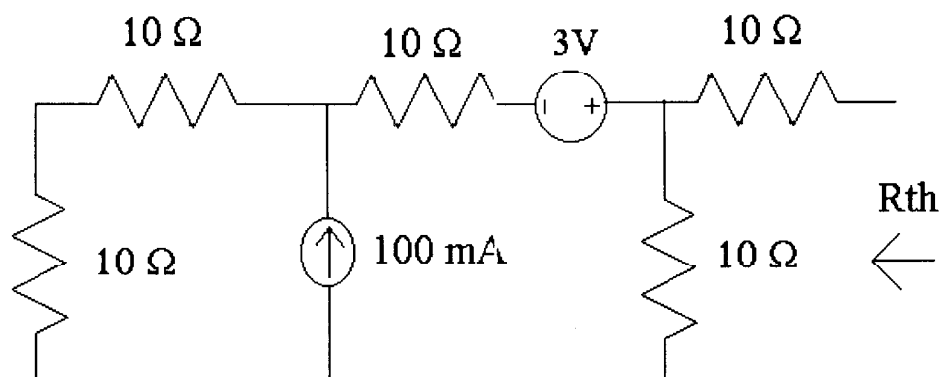


Figure 4-c.

a.

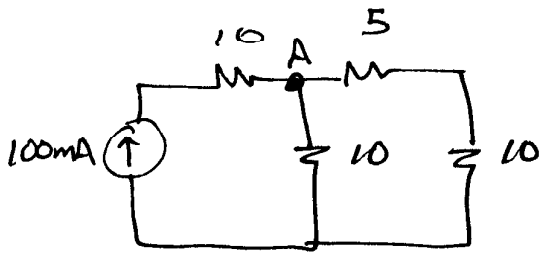


$$-100 \text{ mA} + \frac{A}{10} + \frac{A}{15} = 0$$

$$A = \frac{3}{5} \text{ V}$$

$$V_o = \frac{10}{15} A = \underline{0.4 \text{ V}}$$

b.

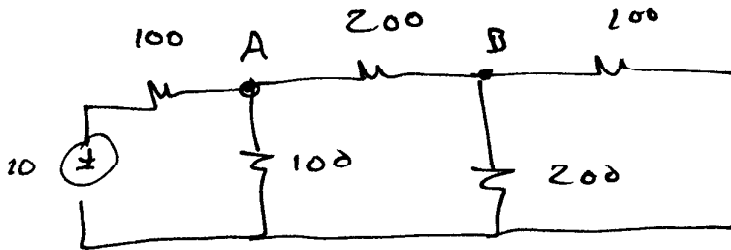



$$\frac{A-10}{100} + \frac{A}{100} + \frac{A-B}{200} = 0 \Rightarrow 3A - B = 20$$

$$\frac{B-A}{200} + \frac{B}{200} + \frac{B}{400} = 0 \Rightarrow -A + 4B = 0$$

$$B = 1.0526 \text{ V}$$


$$I_o = B/100 = \underline{10.52 \text{ mA}}$$

c.

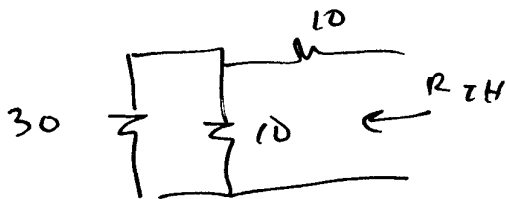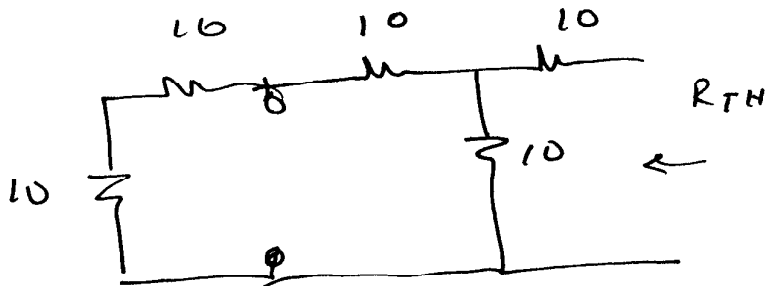

$$\underline{R_{TH} = 17.5 \Omega}$$

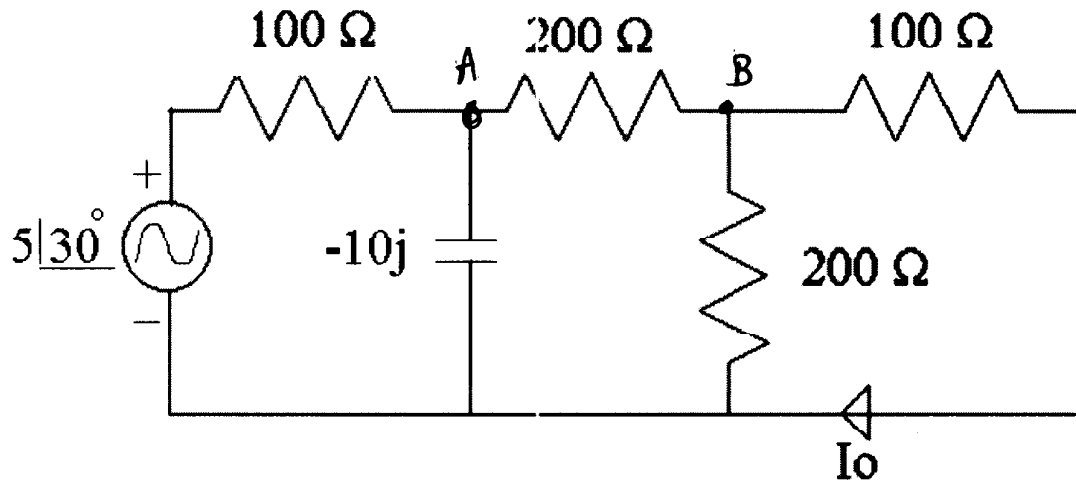5. [13] Find  $I_o$  in the following circuit



$$\frac{A - 5 \angle 30^\circ}{100} + \frac{A}{-10j} + \frac{A - B}{200} = 0$$

$$\frac{B - A}{200} + \frac{B}{200} + \frac{B}{100} = 0$$

$$\begin{bmatrix} .015 + .1j & -.005 \\ -.005 & .02 \end{bmatrix} \begin{bmatrix} A \\ B \end{bmatrix} = \begin{bmatrix} \frac{5 \angle 30^\circ}{100} \\ 0 \end{bmatrix}$$

$$B = .123835 \angle -52.1709^\circ \text{ V}$$

$$I_o = B/100 = 1.238 \angle -52.1709^\circ \text{ mA}$$